

# Experiment 4 - Accelerator and Wrappers

Mohammad Amin Alinejad- 810199463 / Amirali Shahriary- 810100173

**Abstract**— In this experiment, we are going to design an Exponential Accelerator Wrapper. For this design we are going to plan exponential engine, Accelerator wrapper and its controller, then perform our full design on Quartus environment that help us implement this Accelerator on FPGA and finally watch the results on FPGA board.

**Keywords**— SoC, CP, Accelerator, Exponential Engine, handshaking in an SoC, Exponential Accelerator Wrapper, CPU, ROM, FPGA

## I. INTRODUCTION

System on Chip is an integrated circuit that integrates multiple components including digital, analog, hardware, and software programs all in a single chip. The main core of an SoC is a processor that handles different computational tasks within the system. In addition to the processor, the system includes memory, Input/Output ports, and accelerators. accelerators are dedicated computation units that usually execute one specific task. This single task needs a smaller and less complicated datapath which leads to a high frequency of operation for the accelerators. This is contrary to CPUs in which millions of operations must be executed within a fixed time interval. This imposes a low frequency of operation for CPUs.

 


Fig.1 Block diagram of a typical integrated circuit

## II. EXPONENTIAL ENGINE

this module receives a 16-bit input "x" and generates a 16-bit output "Fractionalpart" and 2-bit "Integerpart". The accelerator starts working with a complete pulse on the signal "start" and when the computation is completed signal "done" will be sent to the processor to acknowledge it.

code examination by running Modelsim simulation:

maximum of value that can be run is  $2^{16}=65536$  so when we want to give value to e we should divide it by the maximum capacity( $2^{16}$ ).

 


Fig.2 Block diagram of exponential accelerator

We simulated the code with 3 values of  $x = 8064, 2444, 27020, 508$ . The Verilog description for calculation of (e) was given, the test bench code is below.

```
1 `timescale 1ns/1ns
2 module exponent_TB();
3   reg clk = 1'b0, rst = 1'b0, start=1'b0;
4   wire done;
5   reg [15:0] data_in;
6   wire [1:0] int_part;
7   wire [15:0] frac_part;
8   exponential_crtl(clk,rst,start, data_in, done, int_part, frac_part);
9   always #5 clk = ~clk;
10  initial begin
11    #200 data_in = 16'b0001111110000000;
12    #50 start = 1'b1;
13    #50 start = 1'b0;
14    #200 data_in = 16'b0000100110001100;
15    #50 start = 1'b1;
16    #50 start = 1'b0;
17    #200 data_in = 16'b0110100110001100;
18    #50 start = 1'b1;
19    #50 start = 1'b0;
20    #200 data_in = 16'b0000000111111100;
21    #50 start = 1'b1;
22    #50 start = 1'b0;
23    #1000 $stop;
24  end
25 endmodule
```

Fig.3 Verilog description for the test bench of accelerator.

 


Fig.4 Value of Exponential accelerator for all the modes.

The calculations for each mode are listed below

$$1) \quad x = 8064, \quad 8064/2^{16} \approx 0.123046$$

$$e^{0.123046} \approx 1.130936$$

Output shown as shown in figure is 8577

$$8577/2^{16} \approx 0.1308746$$

As it turns out, the answer is almost equal to the expected output.

$$2) x = 2444, 2444/2^{16} \approx 0.037292$$

$$e^{0.037292} \approx 1.037996$$

Output shown as shown in figure is 2486

$$2486/2^{16} \approx 0.037933$$

As it turns out, the answer is almost equal to the expected output.

$$3) x = 27020, 27020/2^{16} \approx 0.412292$$

$$e^{0.412292} \approx 1.51028$$

Output shown as shown in figure is 33435

$$33435/2^{16} \approx 0.510176$$

As it turns out, the answer is almost equal to the expected output.

$$4) x = 508, 508/2^{16} \approx 0.00775146$$

$$e^{0.00775146} \approx 1.007751$$

Output shown as shown in figure is 506

$$506/2^{16} \approx 0.00772094$$

As it turns out, the answer is almost equal to the expected output.

Some of experiment components & controller Verilog description:

```

1 module shift_reg(input clk, rst, ld, sh_en, input [15:0] vi, output reg [15:0] eng_x);
2
3     always @(posedge clk, posedge rst) begin
4         if(rst == 1'b1)
5             eng_x <= 16'b0;
6         else if(ld == 1'b1)
7             eng_x <= vi;
8         else if(sh_en == 1'b1)
9             eng_x <= {eng_x[14:0], 1'b0};
10    end
11 endmodule

```

Fig.5 Verilog description for shift register.

 


Fig.6 waveform output for shift register.

```

1 module shift_comb(input [1:0] ui, input [17:0] vi, output reg [20:0] wr_data);
2
3     always @(ui, vi) begin
4         case (ui)
5             2'b00 : wr_data <= {3'b0, vi};
6             2'b01 : wr_data <= {2'b0, vi, 1'b0};
7             2'b10 : wr_data <= {1'b0, vi, 2'b0};
8             2'b11 : wr_data <= {vi, 3'b0};
9         endcase
10    end
11 endmodule

```

Fig.7 Verilog description for combinational shift.

 


Fig.8 waveform output for combinational shift register.

```

module controller(input clk,rst,start,co,
                  output reg done, zx,initx,ldx, zt,initz,ldt, zr,initr,ldr, zc,ldc,enc, s);
    reg [2:0] ps, ns;
    parameter [2:0]
    Idle = 0, Initialization = 1, Begin = 2, Mult1 = 3, Mult2 = 4, Add=5;
    always@(ps,co,start)begin
        ns = Idle;
        case(ps)
            Idle:
                ns = (start)? Initialization : Idle;
            Initialization:
                ns = (start)? Initialization : Begin;
            Begin:
                ns = Mult1;
            Mult1:
                ns = Mult2;
            Mult2:
                ns = Add;
            Add:
                ns = (co)? Idle : Mult1;
        endcase
    end
    always@(ps,co,start)begin
        done = 1'b0; zx = 1'b0; initx = 1'b0; ldx = 1'b0; zt = 1'b0; initz = 1'b0; ldt = 1'b0;
        zr = 1'b0; initr = 1'b0; ldr = 1'b0; zc = 1'b0; ldc = 1'b0; enc = 1'b0; s = 1'b0;
        case(ps)
            Idle:begin
                zx = 1'b1;
                zt = 1'b1;
                //zr = 1'b1;
                zc = 1'b1;
                done = 1'b1;
            end
            Initialization:begin
                ldx = 1'b1;
            end
            Begin:begin
                initr = 1'b1;
                initz = 1'b1;
            end
            Mult1:begin
                s = 1'b0;
                ldt = 1'b1;
            end
            Mult2:begin
                s = 1'b1;
                ldt = 1'b1;
            end
            Add:begin
                enc = 1'b1;
                ldr = 1'b1;
            end
        endcase
    end
    end
    always@(posedge clk,posedge rst)begin
        if(rst == 1'b1)
            ps <= Idle;
        else
            ps <= ns;
        end
    end
endmodule

```

Fig.9 controller Verilog description.

As shown in the figure below, The maximum frequency that this exponential calculator can operate is 109.39MHz which we got access to from Fmax summary.

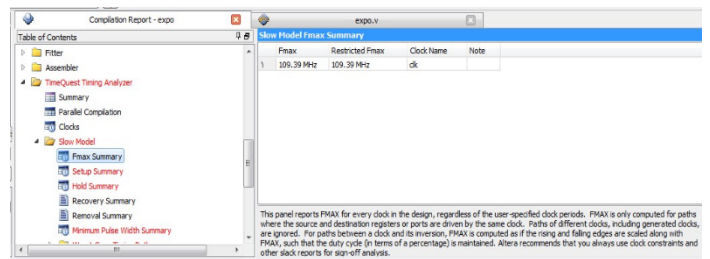


Fig.10 Fmax of Exponential Engine.

### III. EXPONENTIAL ACCELERATOR WRAPPER

Since the accelerator data will be accessed before and after completing CPU task, the data has to be stored in memory elements in the accelerator wrapper when CPU is

 


Fig.11 Exponential accelerator wrapper

busy with other works. The memory element required in this experiment is an input ROM for storing the input data.

The controller in this wrapper is responsible for generating the "start" signal for exponential engine and the address of each input data reading from the input ROM. The exponential engine should start each calculation when the previous one is completely done. Although the accelerator is working with a higher frequency than the processor, for the handshaking signals of "start" and "done" the accelerator have to wait for the processor to send and receive these signals with its low frequency. This imposes some timing overhead to the accelerator and hence performance reduction. In order to use this free time, the accelerator can calculate multiple exponential values. One of the applications that makes use of such multi-value exponential calculation is an activation function in Deep Neural Networks (DNN).

#### IV. IMPLEMENTING ACCELERATOR ON FPGA

By using mega wizard unit, we declare a FIFO unit. FIFO is a group of register which we can store data and it has both read and write option.

The specific option of FIFO is that the reading data are sorted as they entered into the FIFO unit.

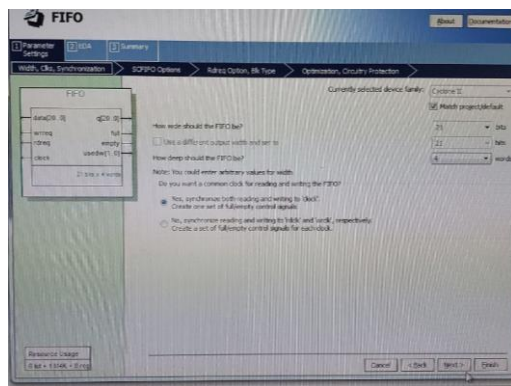


Fig.12 Creating FIFO.

In this part, we are about to connect the main circuit into the FIFO unit and one-pulsar. After that we define the inputs and outputs to plan them in pin planner.

 


Fig.13 schematic of the circuit.

To map the circuit on device we need pin assignment using Cyclone EP2C20F484C7 manual.

 


Fig.14 Pin assignment top view.

Node Name	Direction	Location	I/O Bank	WEP Group	Filter Location	I/O Standard	Reserved	Current Strength	Differential Pair
done	Output	PP1_U11	6	BS_N1	PP1_U11	3.3V LV (default)		24mA (default)	
empty	Output	PP1_U11	6	BS_N1	PP1_U11	3.3V LV (default)		24mA (default)	
key	Input	PP1_U11	6	BS_N1	PP1_U11	3.3V LV (default)		24mA (default)	
out_fifo[20]	Output	PP1_U11	6	BS_N1	PP1_U11	3.3V LV (default)		24mA (default)	
out_fifo[19]	Output	PP1_U11	6	BS_N1	PP1_U11	3.3V LV (default)		24mA (default)	
out_fifo[18]	Output	PP1_U11	6	BS_N1	PP1_U11	3.3V LV (default)		24mA (default)	
out_fifo[17]	Output	PP1_U11	6	BS_N1	PP1_U11	3.3V LV (default)		24mA (default)	
out_fifo[16]	Output	PP1_U11	6	BS_N1	PP1_U11	3.3V LV (default)		24mA (default)	
out_fifo[15]	Output	PP1_U11	6	BS_N1	PP1_U11	3.3V LV (default)		24mA (default)	
out_fifo[14]	Output	PP1_U11	6	BS_N1	PP1_U11	3.3V LV (default)		24mA (default)	
out_fifo[13]	Output	PP1_U11	6	BS_N1	PP1_U11	3.3V LV (default)		24mA (default)	
out_fifo[12]	Output	PP1_U11	6	BS_N1	PP1_U11	3.3V LV (default)		24mA (default)	
out_fifo[11]	Output	PP1_U11	6	BS_N1	PP1_U11	3.3V LV (default)		24mA (default)	

Node Name	Direction	Location	I/O Bank	WEP Group	Filter Location	I/O Standard	Reserved	Current Strength	Differential Pair
push_button	Input	PP1_U11	6	BS_N1	PP1_U11	3.3V LV (default)		24mA (default)	
out_fifo[10]	Output	PP1_U11	6	BS_N1	PP1_U11	3.3V LV (default)		24mA (default)	
out_fifo[9]	Output	PP1_U11	6	BS_N1	PP1_U11	3.3V LV (default)		24mA (default)	
out_fifo[8]	Output	PP1_U11	6	BS_N1	PP1_U11	3.3V LV (default)		24mA (default)	
out_fifo[7]	Output	PP1_U11	6	BS_N1	PP1_U11	3.3V LV (default)		24mA (default)	
out_fifo[6]	Output	PP1_U11	6	BS_N1	PP1_U11	3.3V LV (default)		24mA (default)	
out_fifo[5]	Output	PP1_U11	6	BS_N1	PP1_U11	3.3V LV (default)		24mA (default)	
out_fifo[4]	Output	PP1_U11	6	BS_N1	PP1_U11	3.3V LV (default)		24mA (default)	
out_fifo[3]	Output	PP1_U11	6	BS_N1	PP1_U11	3.3V LV (default)		24mA (default)	
out_fifo[2]	Output	PP1_U11	6	BS_N1	PP1_U11	3.3V LV (default)		24mA (default)	
out_fifo[1]	Output	PP1_U11	6	BS_N1	PP1_U11	3.3V LV (default)		24mA (default)	
push_button	Input	PP1_U11	6	BS_N1	PP1_U11	3.3V LV (default)		24mA (default)	

Node Name	Direction	Location	I/O Bank	WEP Group	Filter Location	I/O Standard	Reserved	Current Strength	Differential Pair
push_button	Input	PP1_U11	6	BS_N1	PP1_U11	3.3V LV (default)		24mA (default)	
key	Input	PP1_U11	6	BS_N1	PP1_U11	3.3V LV (default)		24mA (default)	
start	Input	PP1_U11	6	BS_N1	PP1_U11	3.3V LV (default)		24mA (default)	
stop	Input	PP1_U11	6	BS_N1	PP1_U11	3.3V LV (default)		24mA (default)	
data_in	Input	PP1_U11	6	BS_N1	PP1_U11	3.3V LV (default)		24mA (default)	
data_out	Output	PP1_U11	6	BS_N1	PP1_U11	3.3V LV (default)		24mA (default)	
ledg1	Output	PP1_U11	6	BS_N1	PP1_U11	3.3V LV (default)		24mA (default)	
ledg6	Output	PP1_U11	6	BS_N1	PP1_U11	3.3V LV (default)		24mA (default)	
ledg7	Output	PP1_U11	6	BS_N1	PP1_U11	3.3V LV (default)		24mA (default)	
data_in	Input	PP1_U11	6	BS_N1	PP1_U11	3.3V LV (default)		24mA (default)	
data_out	Output	PP1_U11	6	BS_N1	PP1_U11	3.3V LV (default)		24mA (default)	
push_button	Input	PP1_U11	6	BS_N1	PP1_U11	3.3V LV (default)		24mA (default)	

Fig.15,16&17 Pin assignment.

We assign push button of one-pulsar into Key0. To declare done, empty and full signals we use LEDG1, LEDG6 and LEDG7 respectively.

The output result will be seen on LEDRs and initialization of  $V_i$  and  $U_i$  will be done on SWs.

After this pin planning process, it's time to run the design and investigate the results.

First, we can watch our chip planner which show us that both logic and memory units are used to implement this design.



 


Fig.18 Chip planner.

We can check the summary report of synthesis too.

Flow Summary	
Flow Status	Successful - Sun May 07 04:47:16 2023
Quartus II 64-Bit Version	12.1 Build 177 11/07/2012 53 Web Edition
Revision Name	final_design
Top-level Entity Name	final_design
Family	Cyclone II
Device	EP2K10K10-10
Timing Models	Final
Total logic elements	172 / 18,752 (< 1 %)
Total combinational functions	169 / 18,752 (< 1 %)
Dedicated logic registers	84 / 18,752 (< 1 %)
Total registers	84
Total pins	37 / 315 (12 %)
Total virtual pins	0
Total memory bits	84 / 239,616 (< 1 %)
Embedded Multiplier 9-bit elements	2 / 52 (4 %)
Total PLLs	0 / 4 (0 %)

Fig.19 Flow summary of synthesis.

After compiling the project, we run it on the FPGA. In the following pertaining images the implementation and testing can be seen.

 


Fig.20 Accelerator and Wrappers circuit.

As it can be seen, at first the empty and done signals are active. After 1-0-1 pulse on start, the process will be started and with each pulse on push-button, we can see the output result on LEDRs. We showed the 10 most significant bits of exponential result on FPGA.

For initializing the  $V_i$ s, we fulfill it with 10101 and its concatenated form is 0001010100000000.

As we define this as a input data, our power numbers will be 0.081, 0.162, 0.324 and 0.648.

Now we are going to calculate the result and show it on FPGA.

$$e^{0.081} \approx 1.085$$

$$00001.00010101100101100 \approx 1.085$$

 


Fig.21 First step of showing result.

$$e^{0.162} \approx 1.187$$

$$00001.0010110110001010 \approx 1.187$$

 


Fig.22 Second step of showing result.

$$e^{0.324} \approx 1.388$$

$$00001.0110001100110010 \approx 1.388$$

 


Fig.23 Third step of showing result.

## II. CONCLUSIONS

In this experiment, we learned how to use a accelerator and wrapper in designing a circuit and learned about the FIFO unit and how it works.

## III. REFERENCES

- [1] Katayoon Basharkhah and Zahra Jahanpeim and Zain Navabi, *Digital Logic Laboratory*, University of Tehran, Fall 1402.